

# Foxx Tone Machine Clone

gaussmarkov

August 16, 2007


<http://gaussmarkov.net/index.php?page=layouts#foxx>

## Notes

SOURCE: <http://generalguitargadgets.com>

The power supply has been augmented by a 100uF bypass capacitor and a 1N4004 diode for polarity reversal protection. These can be omitted if desired.

## Layout

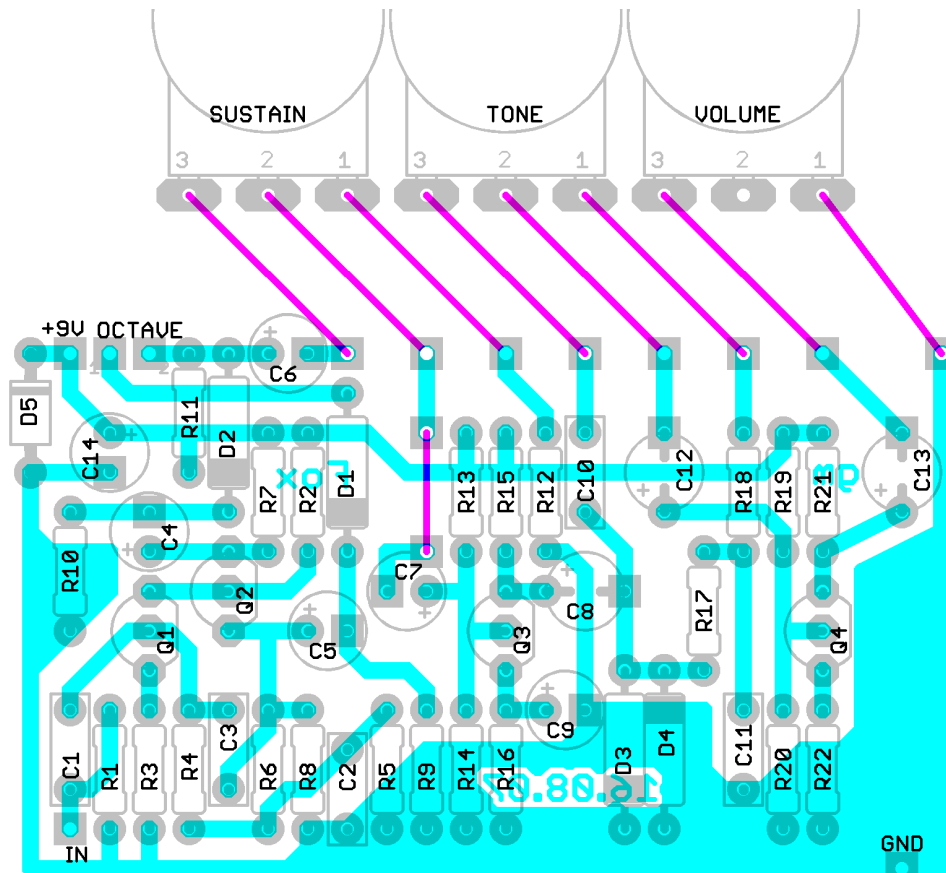

Foxx Tone Machine Clone

16.08.2007 gaussmarkov

# Schematic

